

# Analog to Digital ( A / D ) Converters

# Topics

- A / D Process
- Signal Conditioning
- Type of A / D Converters
- Errors in A / D Converters
- Aliasing

# Course Goals

- We use A / D converters in the laboratory as a general purpose instrument for measuring analog signals (the mixed signal oscilloscope is a digital instrument)
- We use an A / D converter as the primary mechanism for bringing analog signals into a microcomputer for digital signal processing and control purposes
  - In previous case study, we have used an A / D converter to measure the analog voltage from a potentiometer.
  - In the DC motor case study, an A / D converter will measure the analog velocity of the motor using a tachometer.

# A / D Converter Process

An Analog to Digital converter ( A / D ) accepts an analog (continuous in time) electrical signal (a voltage or a current) and converts it to a digital value by:

- Sampling the signal in time
- Quantizing the signal in amplitude

Reference Voltage

$V_{\text{ref}}$

A / D Code

Analog Voltage  
To Measure

$V_a$


Ideal n bit  
A / D  
Converter

$$\text{Digital Code} = (2^n - 1) \frac{V_a}{V_{\text{ref}}}$$

$$\text{Digital Code (10 bits)} = 1023 \frac{V_a}{V_{\text{ref}}}$$


$$\text{Digital Code (8 bits)} = 255 \frac{V_a}{V_{\text{ref}}}$$

# Sampling in Time

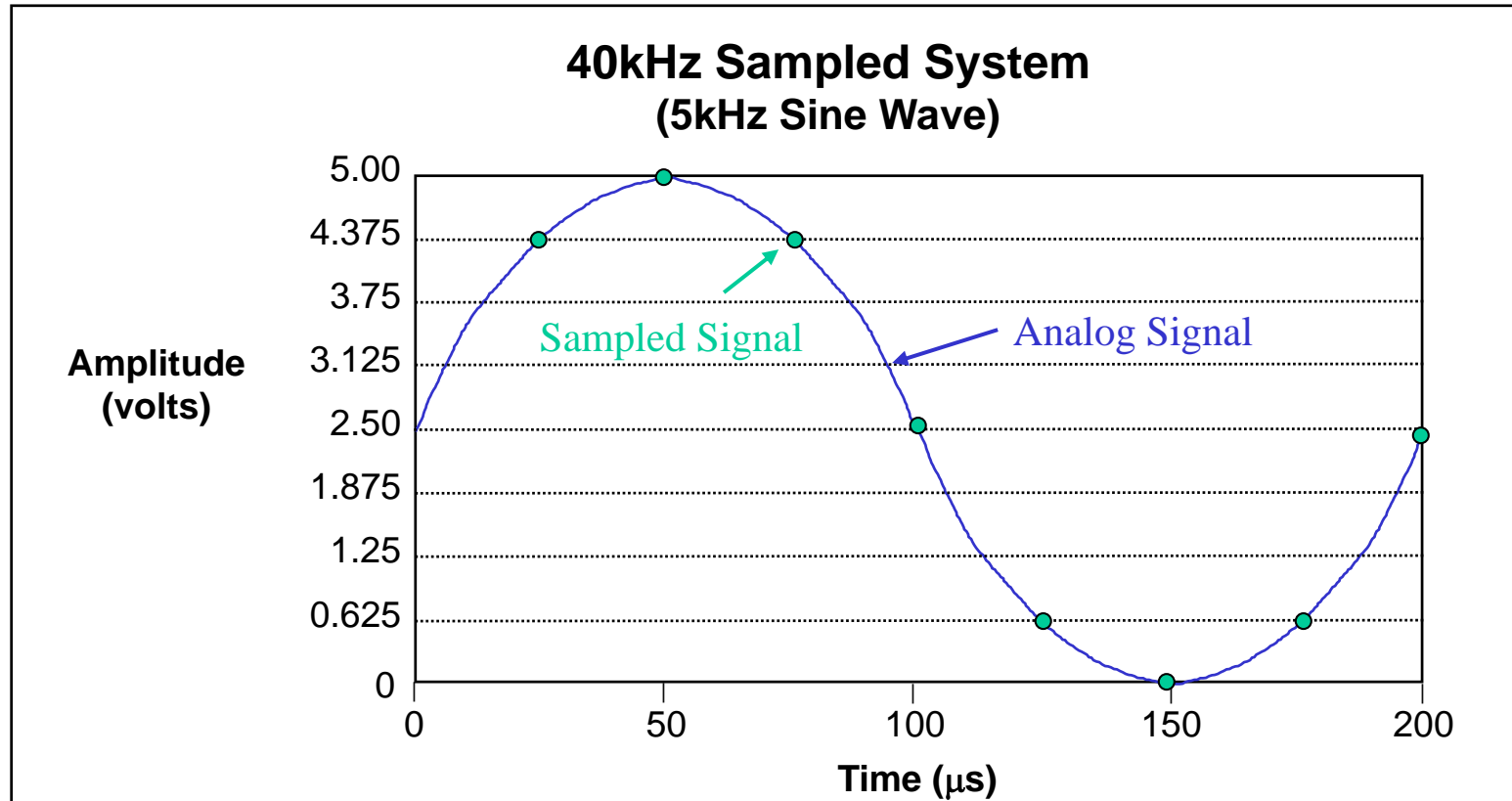

As sampling frequency increases, the digital signal better approximates the analog signal.


# Quantization in Amplitude

 

As resolution increases, the digital signal better approximates the analog signal.

**The maximum quantization error is  $\frac{1}{2}$  the increment size.**

# Quantization Noise

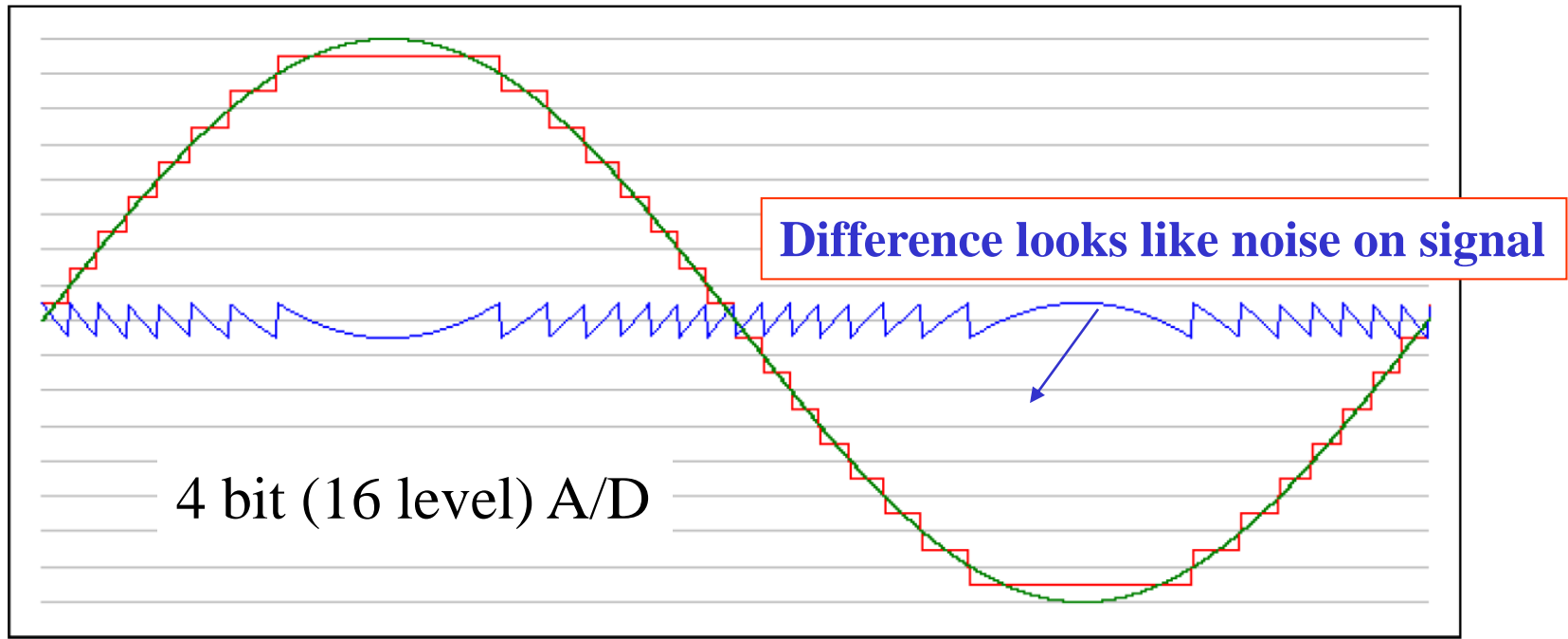


If you assume that the noise is uniformly distributed & uncorrelated with the signal then the rms (root mean square) value of the noise is

$$\frac{1}{\sqrt{12}} \text{ LSB} \quad (\text{that is, the standard deviation of the uniform distribution})$$



# Quantization Noise 16 bit Converter

 

**Green** – analog signal

**Red** – sampled A / D output



**Blue** – noise (difference)

# Digital Signals


Digital signals are **both** sampled in time and quantized in amplitude.

- Sampling in Time Issues
  - Uniform vs. Non-Uniform sampling
  - Sampling frequency
  - Sample time accuracy
- Quantization in amplitude issues
  - Resolution
  - Conversion time
  - Conversion method
 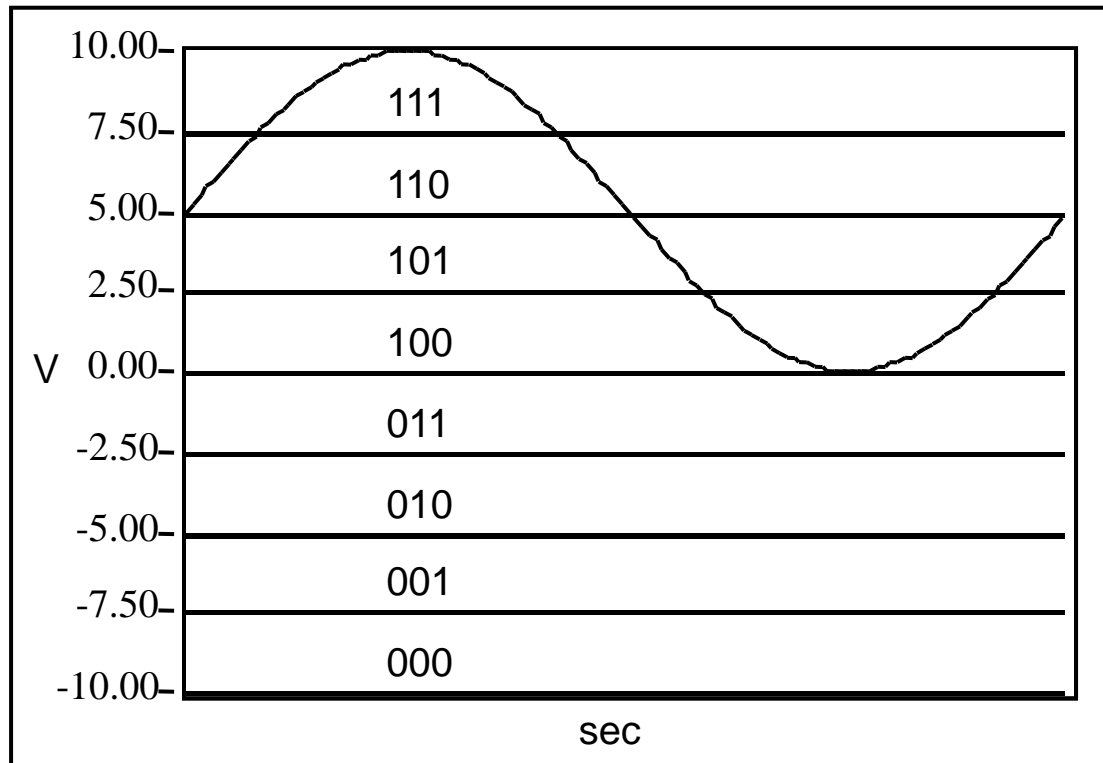
# The optimal resolution depends on the range of signal being measured.



Range = 0 V to 10 V

 


Range = -10 V to +10 V


For Instruments & DAQ boards, the A / D determines the resolution.  
In Microcontrollers, it may be determined by the data word size but can be different (MicroChip has parts with 10 or 12 bit A/D and an 8 bit word).

# Analog World

# Digital World

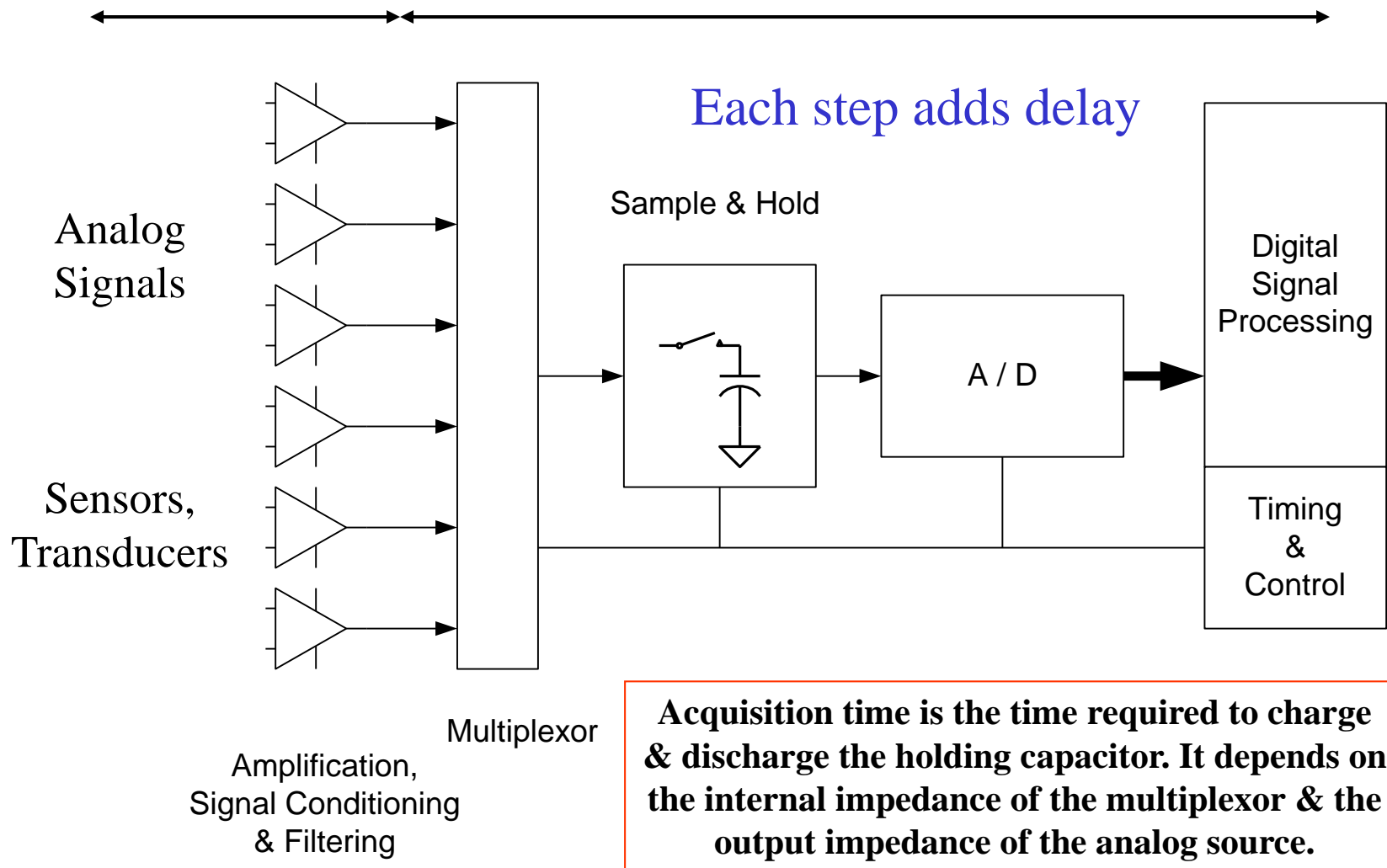
 
# Amplification (or attenuation) sets the range of the analog signal.




From a design perspective, you want to set the analog range to coincide with the range of the A / D.

Too small -> limited detectable range.

Too large -> clipping.

# Code Width Determination

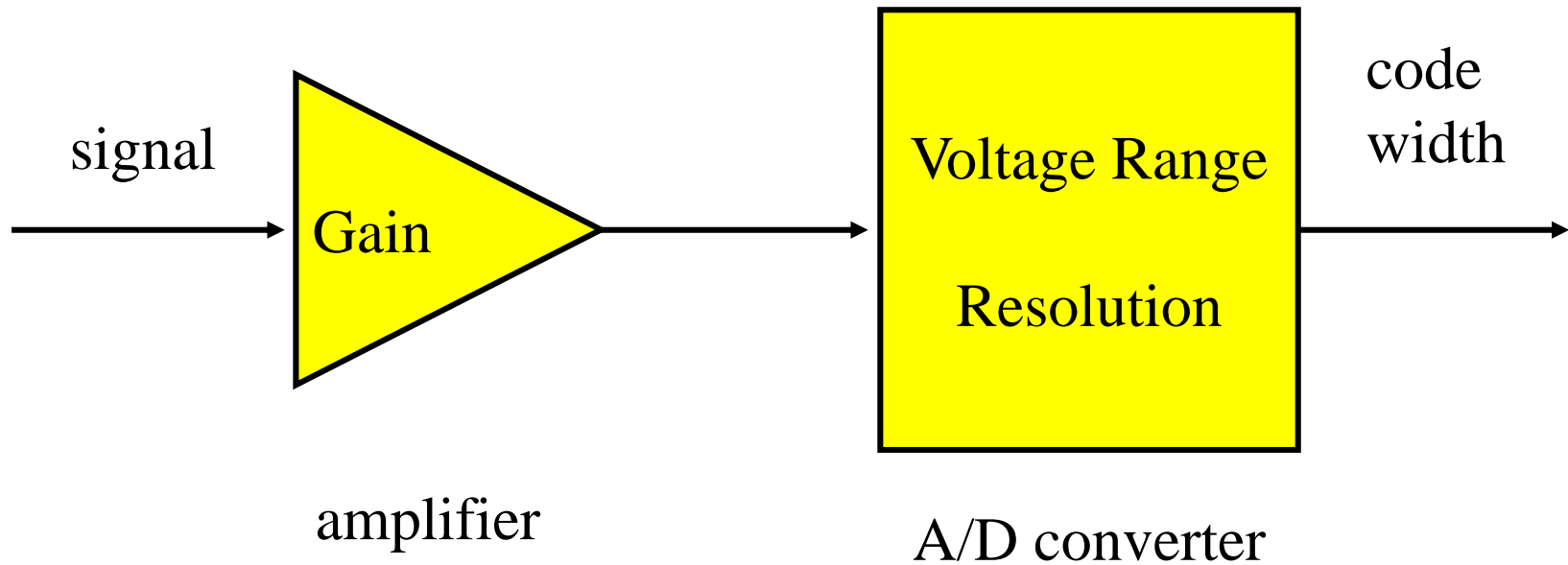

**How much does the signal have to change to produce a 1 bit change in the output of the A/D converter?**

# Detectable limit (code width) with respect to range, gain and resolution

- Resolution, range, and gain determine the smallest detectable change in signal voltage (code width).

$$\text{code width} = \frac{\text{converter range}}{\text{gain} * 2^{\text{resolution}}}$$

- Example: 10-bit converter, range = 0 to 5V, gain = 1

$$\frac{\text{converter range}}{\text{gain} * 2^{\text{resolution}}} = \frac{5}{1 * 2^{10}} = 4.88 \text{ mV}$$

$$\text{Increase range: } \frac{10}{1 * 2^{10}} = 9.76 \text{ mV}$$

$$\text{Increase gain: } \frac{5}{2 * 2^{10}} = 2.44 \text{ mV}$$

# Detectable limit (code width) of Microchip Microcomputer (assuming 8 bits used)

$$\text{code width} = \frac{\text{converter range}}{\text{gain} * 2^{\text{resolution}}}$$

- Example: 8-bit board, range = 0 to 5V, gain = 1

$$\frac{\text{converter range}}{\text{gain} * 2^{\text{resolution}}} = \frac{5}{1 * 2^8} = 19.5 \text{ mV}$$

Increase range is not possible (cannot read 10 V)


$$\text{Increase gain: } \frac{5}{2 * 2^8} = 9.8 \text{ mV}$$



# Signal Conditioning


- Transducer Excitation
  - External voltage or current applied to transducer
  - Provided by signal conditioning hardware
- Linearization
  - Most transducers are not linear
  - Can be done in hardware or software
- Amplification
  - Amplification or Attenuation to span input range
  - Level shifting
- Filtering
  - Remove noise or unwanted signals
  - Remove 60 Hz AC noise from slowly sampled signals
  - Antialiasing filters

# Unipolar or Bipolar

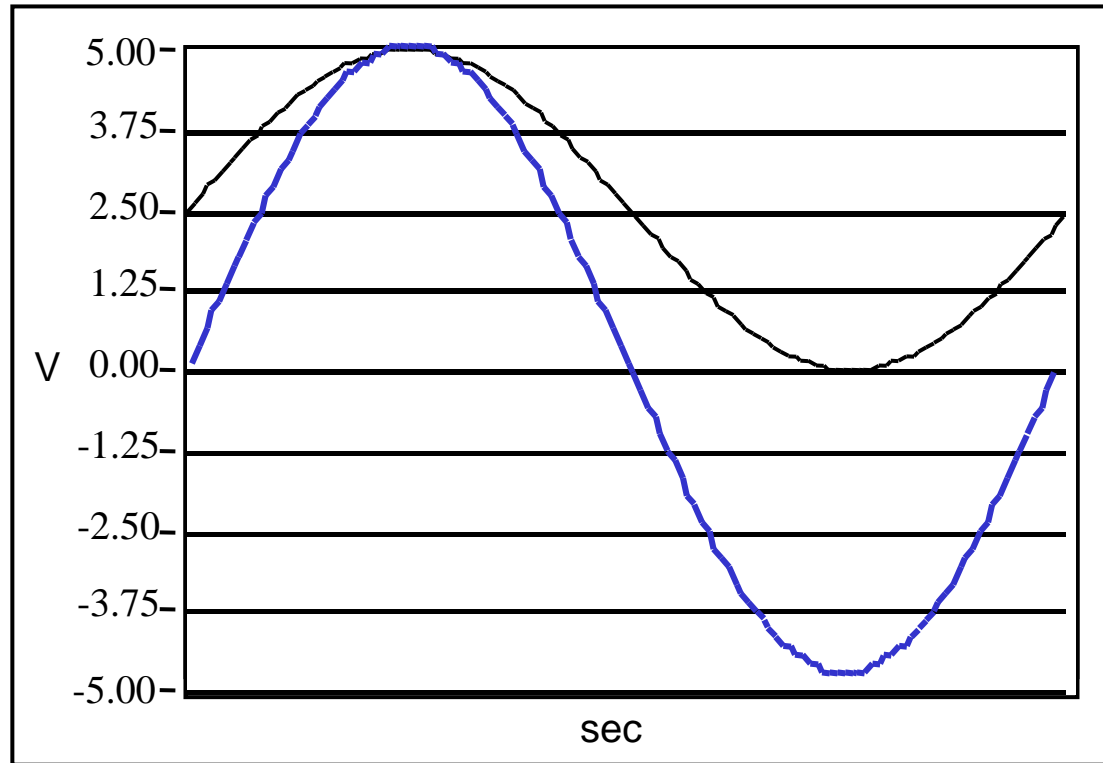

**Microcontroller A / Ds are typically unipolar (0 to 5 Volts) and require level shifting and attenuation of bipolar signals.**
 
# Amplification increases accuracy and improves signal to noise ratio (SNR).





	Signal Voltage	External Amplification	Noise in Lead Wires	DAQ Board Amplification	Digitized Voltage	SNR
Amplify only at DAQ Board	.01 V	None	.001 V	x100	1.1 V	<b>10</b>
Amplify Externally and DAQ Board	.01 V	x10	.001 V	x10	1.01 V	<b>100</b>
Amplify only Externally	.01 V	x100	.001 V	None	1.001 V	<b>1000</b>

# Sample and Hold



- Analog signal is held at a fixed value during the data conversion
- Can be thought of as charging a capacitor
- Sample and Hold (S /H)
  - Sample analog value and charge capacitor to this value
- Track and Hold (T/H)
  - Attach analog signal to capacitor and hold for conversion

# Sample and Hold Control

  
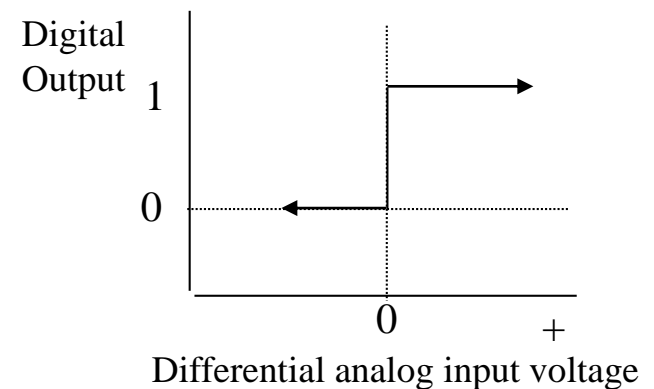 
# A / D Converters

- A fundamental building block of any A/D is a comparator.
- The comparator is really a 1 bit A/D
- It has 2 analog inputs and 1 digital output
- The comparator compares 2 analog signals
  - If the voltage of the + input is greater than the voltage at the – input, the digital output is 1.
  - If the voltage of the - input is greater than the voltage at the + input, the digital output is 0.




# Types of A/D Converters

- Flash
- Successive – Approximation Register
- Multistage
- Integrating
- Sigma - Delta
 
# Flash Converters


- Simultaneous conversion
- Does not require S/H
- Video application
- Very fast
- N bits of resolution requires  $2^n - 1$  comparators
- Accuracy requires precision resistors
- Comparator output called “thermometer code”
- Logic converts thermometer code to normal n-bit binary numbers




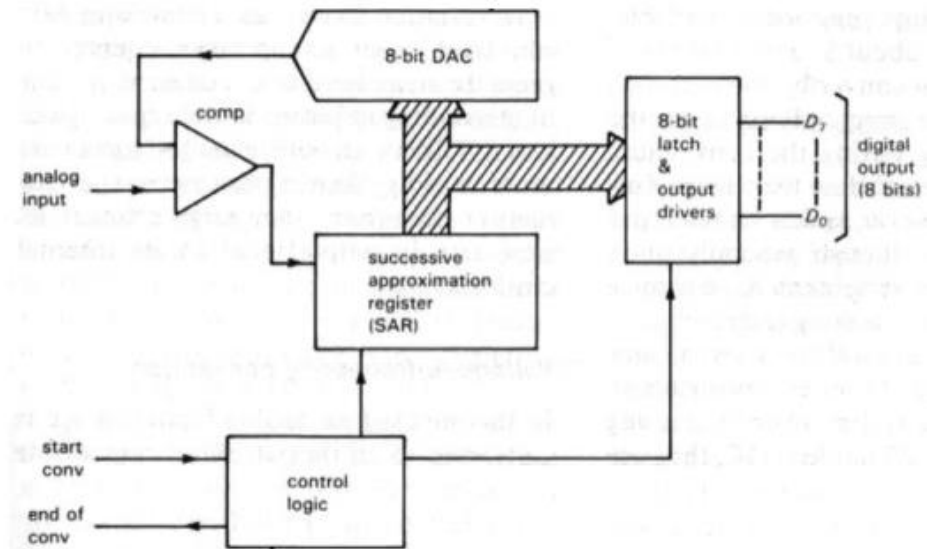
# Successive Approximation Register (SAR) Converters

- Contains a D/A
- Most common electronic A/D
- Low cost
- Good linearity
- SAR sequences the D/A through a series of  $n$  guesses of the analog value which are compared in the comparator




D/A in feedback loop

A/D on MicroChip PIC16F74 is a SAR A/D

# Successive Approximation Concept

8 bit converter

 

Each bit requires one A/D clock cycle (must meet minimum time).  
Two to three additional cycles required for settling.  
Final result must be written to register (requiring time).

# A / D Conversion Steps

- Select the Channel to Convert
- Configure and Enable the A/D
- Wait the Acquisition Time
- Initiate the Conversion
- Wait for the Conversion to Complete (or Enable Interrupt)
- Read the Result


**Timing is still required in C.**

# Multistage

- Higher sample rates at higher resolutions than SAR converters
- Replace comparator with low resolution (4 to 8 bit) flash converter
- Convert upper range and lower range of analog signal in stages
- Adding a S/H or T/H at the input will allow converter to process signals in a pipeline
- Also called a subranging or multipass A/D converter


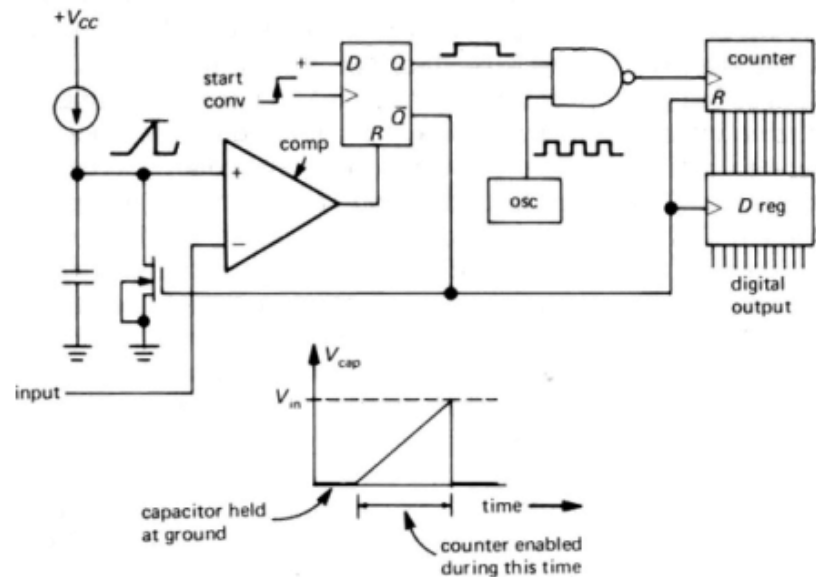
# Integrating

- Low speed
- High resolution
- Voltmeters
- Integrate analog signal until it reaches a certain value
- Record the time required (count pulses)



  
# Dual Slope Integrating


- Time required to integrate in positive and negative direction



# Sigma Delta Converter

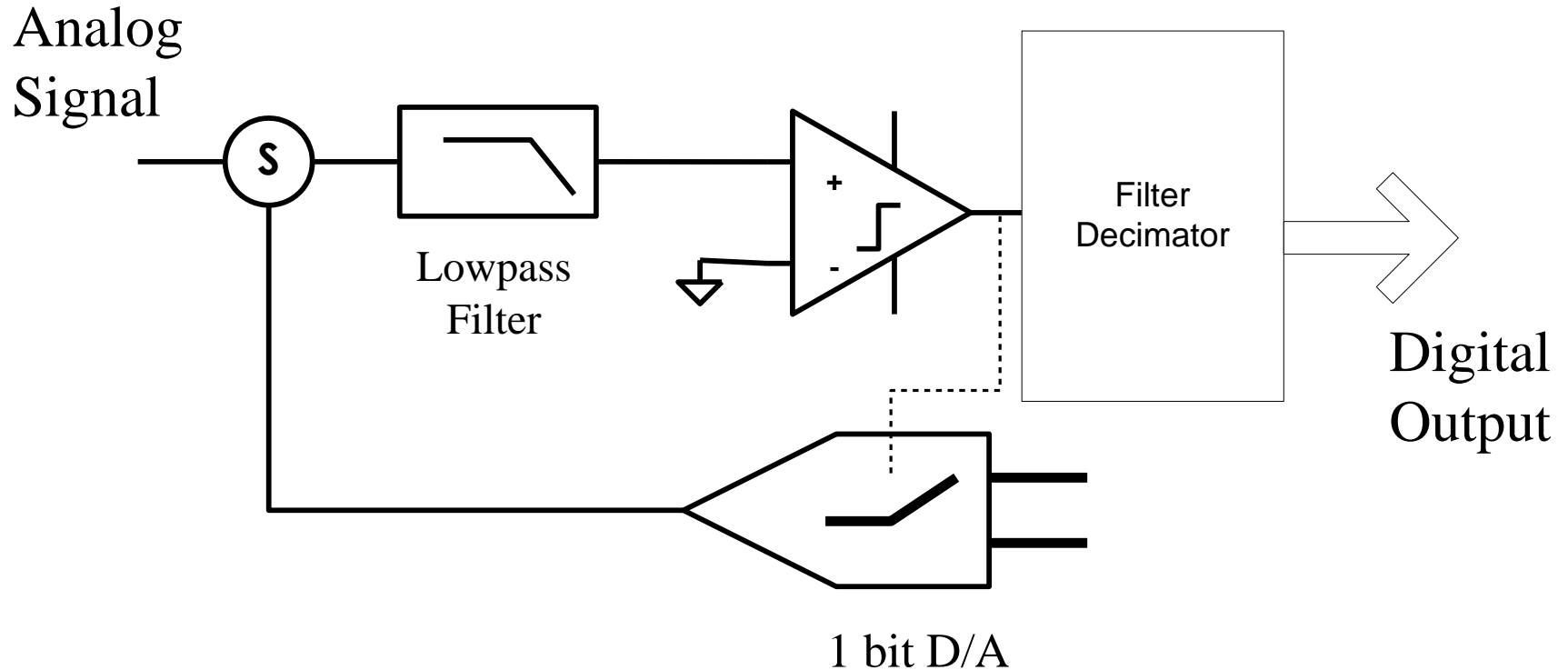

# First Order Sigma Delta Operation

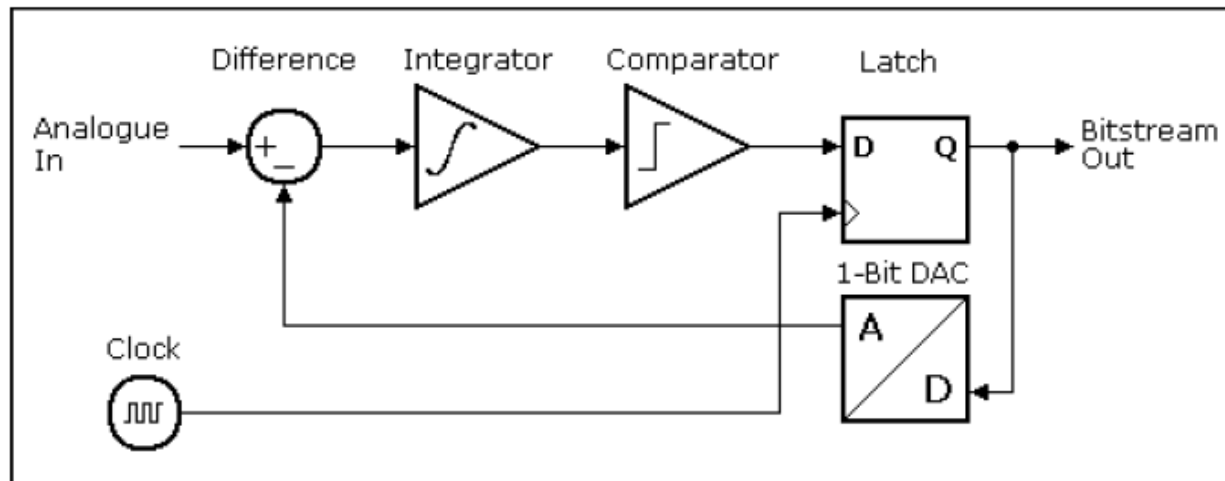

Pulse Proportion  
Modulation  
(PPM) as  
opposed to Pulse  
Code Modulation  
(PCM) for other  
A/Ds

Comparator outputs digital 0 when input  $< 0$   
digital 1 when input  $> 0$


1-bit DAC produces voltage  $V_{\text{ref}}^+$  when input = 1  
voltage  $V_{\text{ref}}^-$  when input = 0




 
# Sigma Delta A/D Signals

clock rate  
shown is 64x  
analog  
frequency

If you want to  
“oversample” a  
20 kHz  
bandwidth  
audio signal at  
48 kHz you  
want clock rate  
 $48 \times 64 \text{ kHz} =$   
3.07 MHz




# A/D Comparison

  

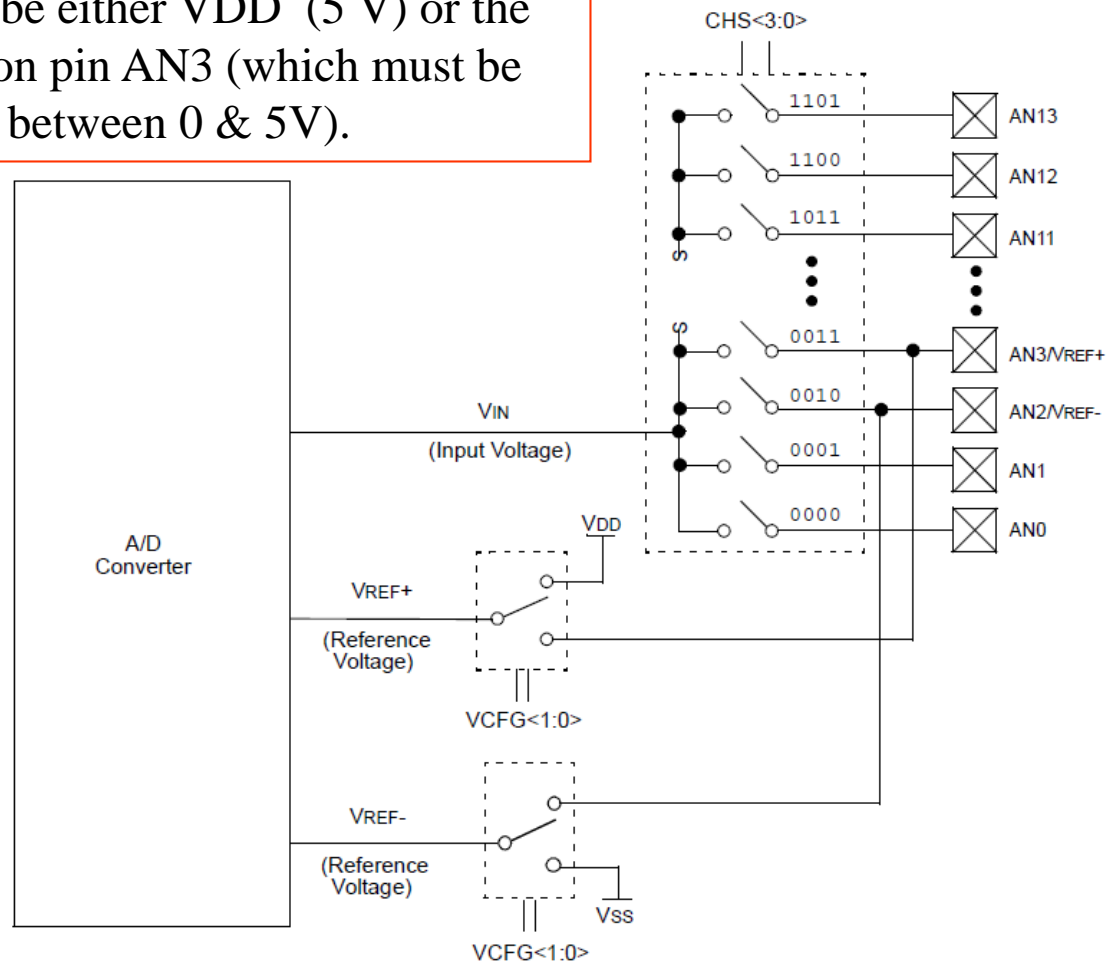
# PIC16F747 A/D Block Diagram

The reference voltage for the A / D can be set to be either VDD (5 V) or the voltage on pin AN3 (which must be between 0 & 5V).



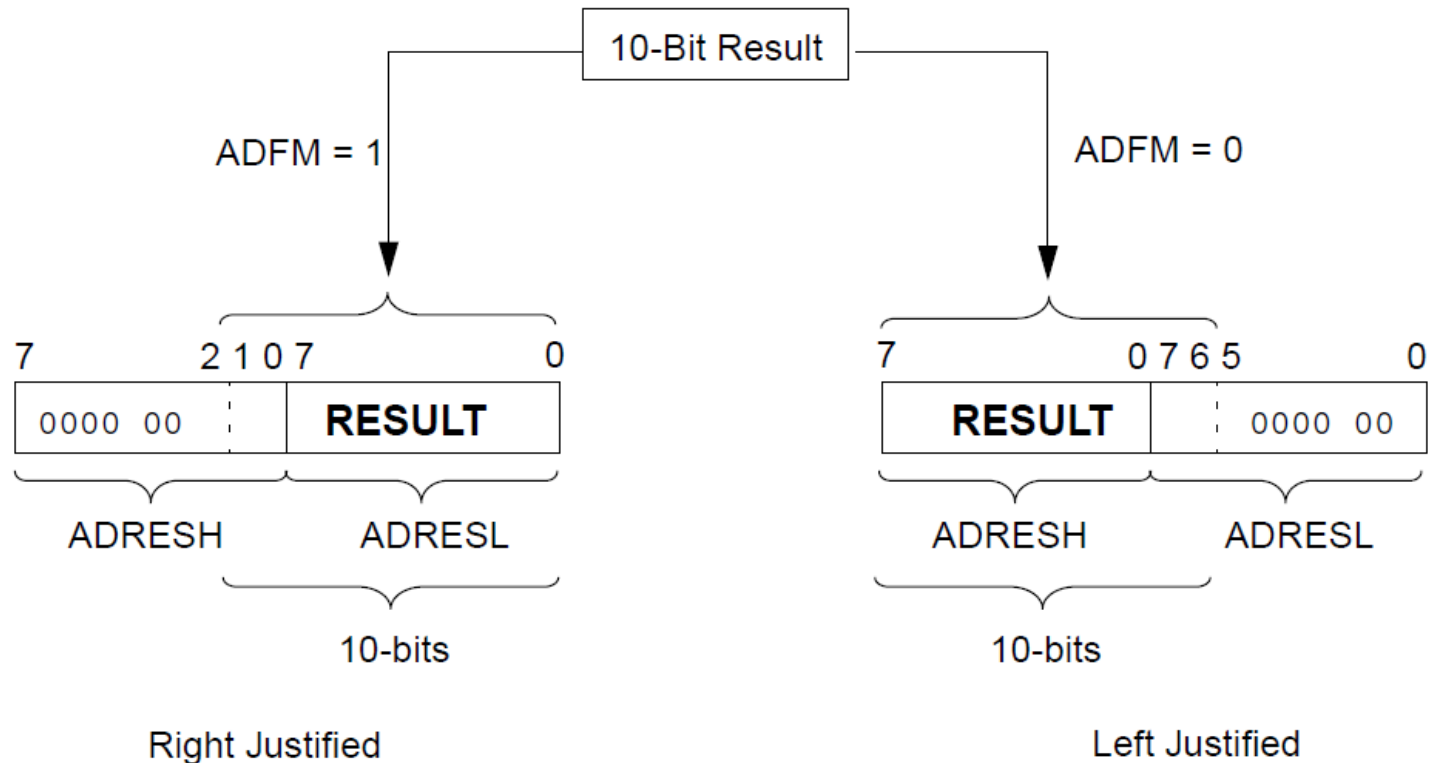
# PIC16F747 A/D Result


The result for the A / D can be either right or left justified depending on the ADFM bit in ADCON1. Should use ADFM == 0 for these case studies.



# PIC16F747 Analog Input Model

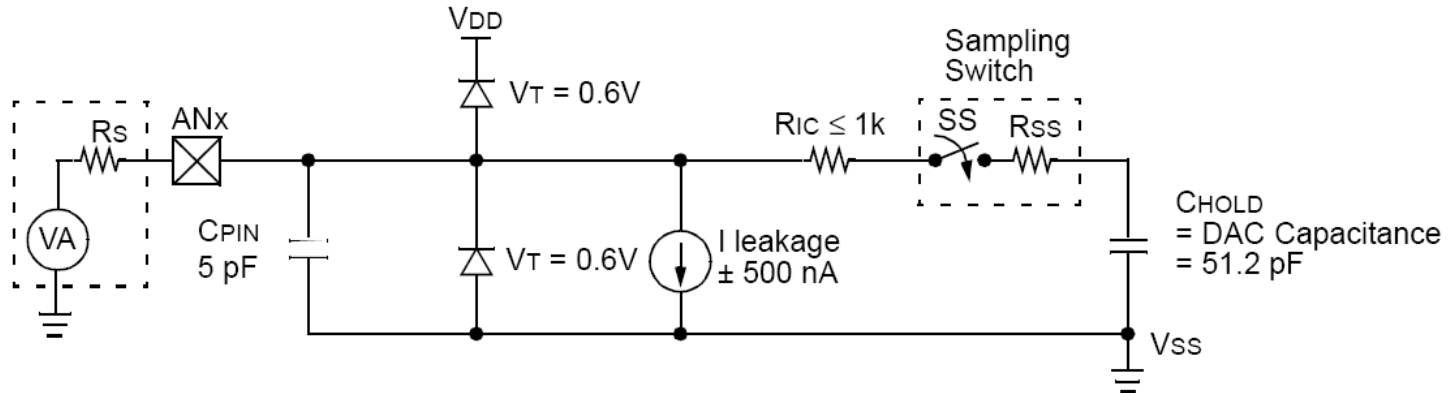

Legend	$C_{PIN}$	= input capacitance
	$V_T$	= threshold voltage
	$I_{leakage}$	= leakage current at the pin due to various junctions
	$R_{ic}$	= interconnect resistance
	$SS$	= sampling switch
	$CHOLD$	= sample/hold capacitance (from DAC)

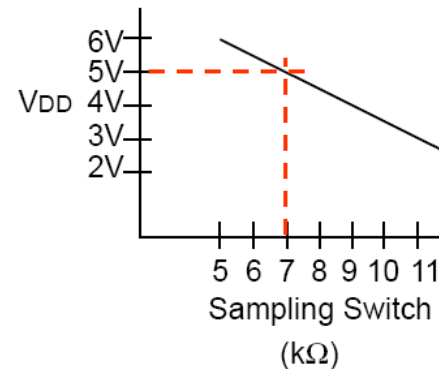

NOTE:  $F_{osc}$  is frequency of the microcomputer oscillator (e.g. 4 MHz)  
 $T_{osc}$  is period of the microcomputer oscillator =  $1 / F_{osc}$  (e.g. 250 nsec)  
 $T_{ins}$  is the instruction cycle period =  $4 \times T_{osc}$  (e.g. 1  $\mu$ sec)

$$\begin{aligned} T_{ACQ} &= \text{Amplifier Settling Time} + \\ &\quad \text{Holding Capacitor Charging Time} + \\ &\quad \text{Temperature Coefficient Time} \\ &= T_{AMP} + T_C + T_{COFF} \end{aligned}$$

$$T_{AMP} + T_C + T_{COFF}$$

$$2 \mu\text{s} + T_C + [(\text{Temperature} - 25^\circ\text{C})(0.05 \mu\text{s}/^\circ\text{C})]$$

$$\text{CHOLD} (\text{RIC} + \text{RSS} + \text{RS}) \ln(1/2047)$$

$$-120 \text{ pF} (1 \text{ k}\Omega + 7 \text{ k}\Omega + 10 \text{ k}\Omega) \ln(0.0004885)$$


$$16.47 \mu\text{s}$$

$$2 \mu\text{s} + 16.47 \mu\text{s} + [(50^\circ\text{C} - 25^\circ\text{C})(0.05 \mu\text{s}/^\circ\text{C})]$$

$$19.72 \mu\text{s}$$


**A/D  
Acquisition  
Time**

# A/D Sample Time

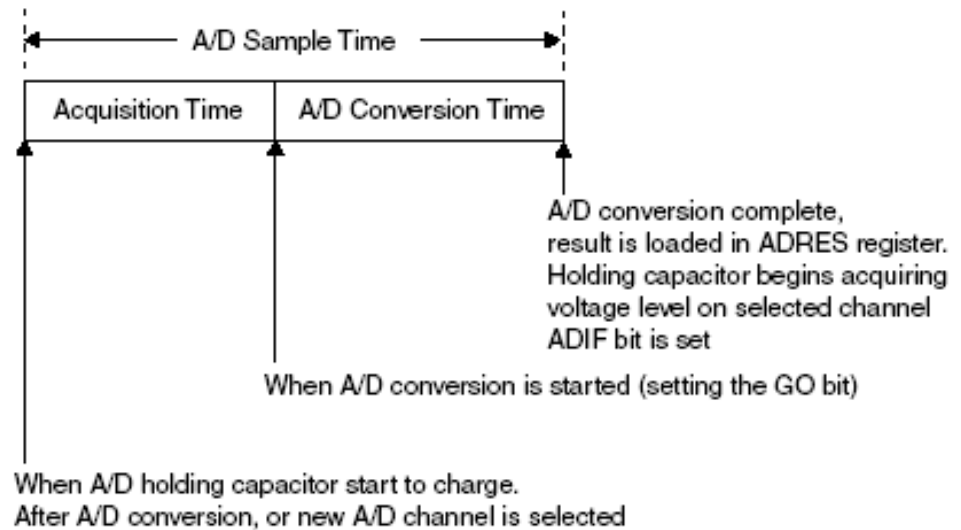

## A / D Conversion Time


**FIGURE 12-4: A/D CONVERSION TAD CYCLES (ACQT<2:0> = 010, TACQ = 4 TAD)**

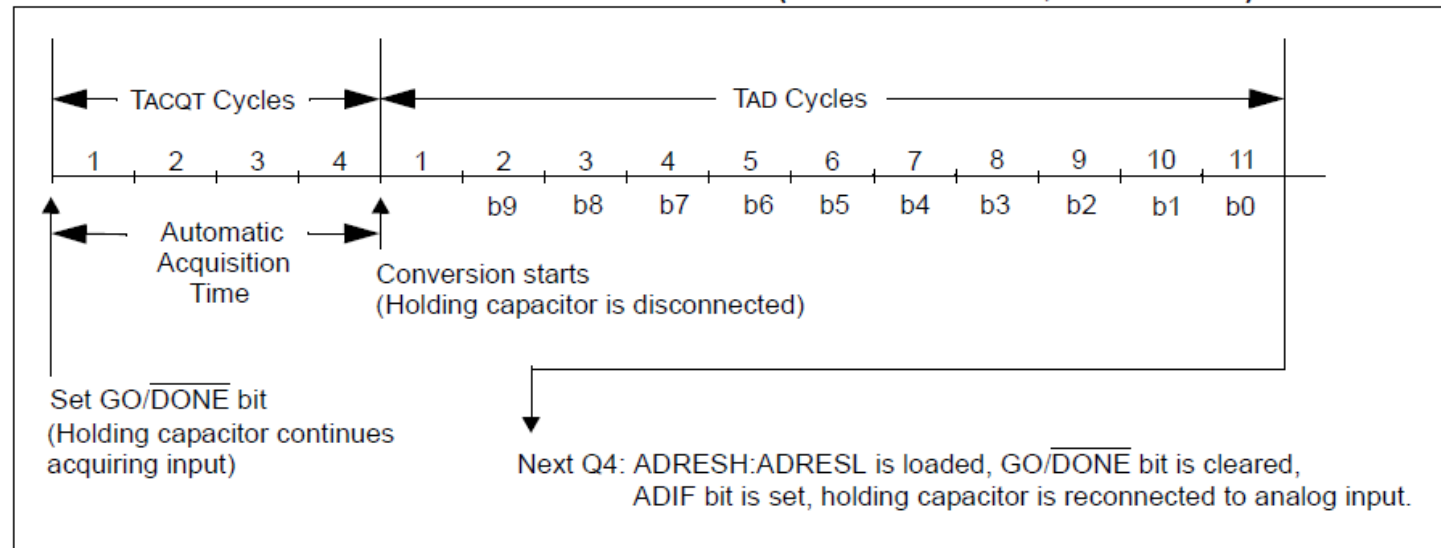

# A/D Sample Time

## A / D Conversion Time Single Channel

FIGURE 12-3: A/D CONVERSION TAD CYCLES (ACQT<2:0> = 000, TACQ = 0)

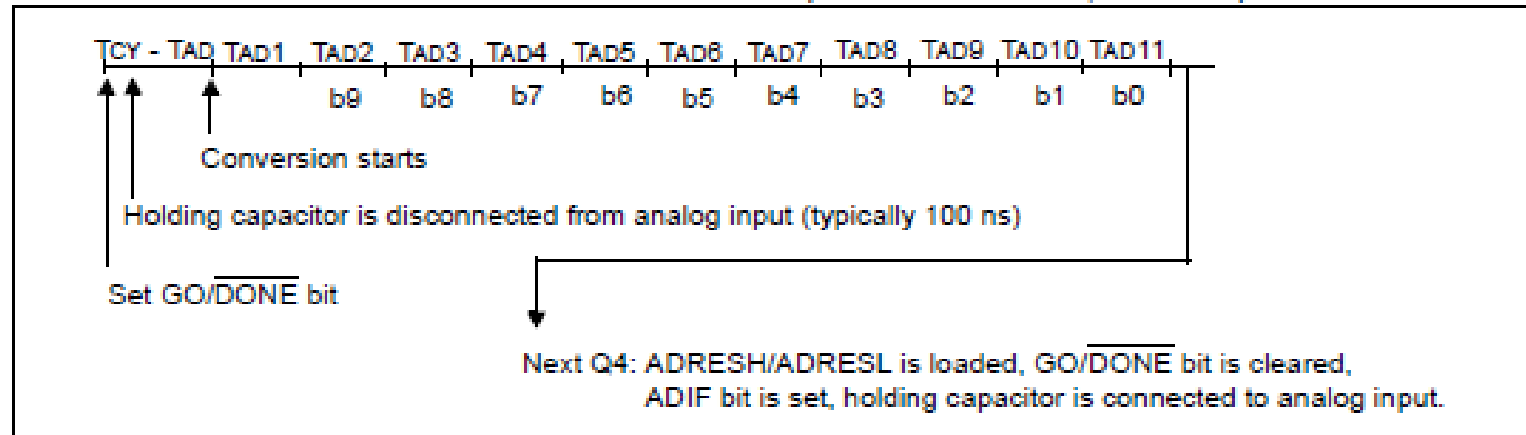



# A/D Sample Time

**A / D  
operates  
slower than  
the CPU**

**TABLE 12-1: TAD vs. MAXIMUM DEVICE OPERATING FREQUENCIES (STANDARD DEVICES (F))**

AD Clock Source (TAD)		Maximum Device Frequency
Operation	ADCS2:ADCS1:ADCS0	
2 TOSC	000	1.25 MHz
4 TOSC	100	2.5 MHz
8 TOSC	001	5 MHz
16 TOSC	101	10 MHz
32 TOSC	010	20 MHz
64 TOSC	110	20 MHz
RC <sup>(1,2,3)</sup>	x11	<b>(Note 1)</b>

# Setting A/D Control Registers ADCON0

bit 7-6

**ADCS1:ADCS0:** A/D Conversion Clock Select bits

If ADCS2 = 0;

000 = FOSC/2

001 = FOSC/8

010 = FOSC/32

011 = FRC (clock derived from an RC oscillation)

If ADCS2 = 1;

00 = FOSC/4

01 = FOSC/16

10 = FOSC/64

11 = FRC (clock derived from an RC oscillation)

PIF 1					PIF 0		
ADCS1	ADCS0	CHS5	CHS4	CHS3	GO/DONE	CHS2	ADON
BWM-0	BWM-0	BWM-0	BWM-0	BWM-0	BWM-0	BWM-0	BWM-0

bit 5-3

**CHS<2:0>:** Analog Channel Select bits

0000 = Channel 00 (AN0)

0001 = Channel 01 (AN1)

0010 = Channel 02 (AN2)

0011 = Channel 03 (AN3)

0100 = Channel 04 (AN4)

0101 = Channel 05 (AN5)<sup>(1)</sup>

0110 = Channel 06 (AN6)<sup>(1)</sup>

0111 = Channel 07 (AN7)<sup>(1)</sup>

1000 = Channel 08 (AN8)

1001 = Channel 09 (AN9)

1010 = Channel 10 (AN10)

1011 = Channel 11 (AN11)

1100 = Channel 12 (AN12)

1101 = Channel 13 (AN13)

111x = Unused

**Note 1:** Selecting AN5 through AN7 on the 28-pin product variant (PIC16F737 and PIC16F767) will result in a full-scale conversion as unimplemented channels are connected to VDD.

bit 2

**GO/DONE:** A/D Conversion Status bit

1 = A/D conversion cycle in progress. Setting this bit starts an A/D conversion cycle. This bit is automatically cleared by hardware when the A/D conversion has completed.

0 = A/D conversion completed/not in progress

bit 1

**CHS<3>:** Analog Channel Select bit (see bit 5-3 for bit settings)

bit 0

**ADON:** A/D Conversion Status bit

1 = A/D converter module is operating

0 = A/D converter is shut-off and consumes no operating current

# Setting A/D Control Registers ADCON1

R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0
ADFM	ADCS2	VCFG1	VCFG0	PCFG3	PCFG2	PCFG1	PCFG0
bit 7						bit 0	

- bit 7 **ADFM**: A/D Result Format Select bit  
1 = Right justified. Six Most Significant bits of ADRESH are read as '0'.  
0 = Left justified. Six Least Significant bits of ADRESL are read as '0'.
- bit 6 **ADCS2**: A/D Clock Divide by 2 Select bit  
1 = A/D clock source is divided by two when system clock is used  
0 = Disabled
- bit 5 **VCFG1**: Voltage Reference Configuration bit 1  
0 = VREF- is connected to VSS  
1 = VREF- is connected to external VREF- (RA2)
- bit 4 **VCFG0**: Voltage Reference Configuration bit 0  
0 = VREF+ is connected to VDD  
1 = VREF+ is connected to external VREF+ (RA3)
- bit 3-0 **PCFG<3:0>**: A/D Port Configuration bits

	AN13	AN12	AN11	AN10	AN9	AN8	AN7	AN6	AN5	AN4	AN3	AN2	AN1	AN0
0000	A	A	A	A	A	A	A	A	A	A	A	A	A	A
0001	A	A	A	A	A	A	A	A	A	A	A	A	A	A
0010	D	A	A	A	A	A	A	A	A	A	A	A	A	A
0011	D	D	A	A	A	A	A	A	A	A	A	A	A	A
0100	D	D	D	A	A	A	A	A	A	A	A	A	A	A
0101	D	D	D	D	A	A	A	A	A	A	A	A	A	A
0110	D	D	D	D	D	A	A	A	A	A	A	A	A	A
0111	D	D	D	D	D	D	A	A	A	A	A	A	A	A
1000	D	D	D	D	D	D	D	A	A	A	A	A	A	A
1001	D	D	D	D	D	D	D	D	A	A	A	A	A	A
1010	D	D	D	D	D	D	D	D	D	A	A	A	A	A
1011	D	D	D	D	D	D	D	D	D	D	A	A	A	A
1100	D	D	D	D	D	D	D	D	D	D	D	A	A	A
1101	D	D	D	D	D	D	D	D	D	D	D	D	A	A
1110	D	D	D	D	D	D	D	D	D	D	D	D	D	A
1111	D	D	D	D	D	D	D	D	D	D	D	D	D	D

Legend: A = Analog input, D = Digital I/O

# Setting A/D Control Registers

## ADCON2

U-0	U-0	R/W-0	R/W-0	R/W-0	U-0	U-0	U-0
—	—	ACQT2	ACQT1	ACQT0	—	—	—
bit 7							bit 0

bit 7-6 **Unimplemented:** Read as '0'

bit 5-3 **ACQT<2:0>:** A/D Acquisition Time Select bits

000 = 0<sup>(1)</sup>

001 = 2 TAD

010 = 4 TAD

011 = 6 TAD

100 = 8 TAD

101 = 12TAD

110 = 16 TAD

111 = 20 TAD

**Note 1:** If the A/D clock source is selected as RC, a time of TCY is added before the A/D clock starts. This allows the **SLEEP** instruction to be executed.

bit 2-0 **Unimplemented:** Read as '0'

# Conversion to Binary

2's complement

Adding an Offset for Monotonic Progression

	+	6	5	4	3	2	1	0
127	0	1	1	1	1	1	1	1
126	0	1	1	1	1	1	1	0
2	0	0	0	0	0	0	1	0
1	0	0	0	0	0	0	0	1
0	0	0	0	0	0	0	0	0
-1	1	1	1	1	1	1	1	1
-2	1	1	1	1	1	1	1	0
-3	1	1	1	1	1	1	0	0
-126	1	0	0	0	0	0	1	0
-127	1	0	0	0	0	0	0	1
-128	1	0	0	0	0	0	0	0


	+	6	5	4	3	2	1	0
127	1	1	1	1	1	1	1	1
126	1	1	1	1	1	1	1	0
2	1	0	0	0	0	0	1	0
1	1	0	0	0	0	0	0	1
0	1	0	0	0	0	0	0	0
-1	0	1	1	1	1	1	1	1
-2	0	1	1	1	1	1	1	0
-3	0	1	1	1	1	1	0	0
-126	0	0	0	0	0	0	1	0
-127	0	0	0	0	0	0	0	1
-128	0	0	0	0	0	0	0	0

# Errors in Conversion

Linearity (slope)  
errors

Non-monotonic  
errors



Nonlinear  
errors

 

# Aliasing

- Nyquist Theorem – sample at greater than twice the rate of the maximum frequency component in the input signal
- Nyquist frequency – half the sampling frequency
- Only possible to recover frequencies at or below Nyquist
- Frequencies above Nyquist will “alias” between DC and Nyquist
- Alias frequency = Absolute Value (closest integer multiple of sampling frequency - input frequency)


# Aliasing Example

  



 
# Preventing Aliasing

- Oversampling
- Use filters designed to eliminate frequencies over Nyquist frequency
- Use combination of both because real-world filters exhibit some roll-off
- Use special antialiasing filters that have sharp roll-off



**Ideal Filter**

 

**Real-World Filter**